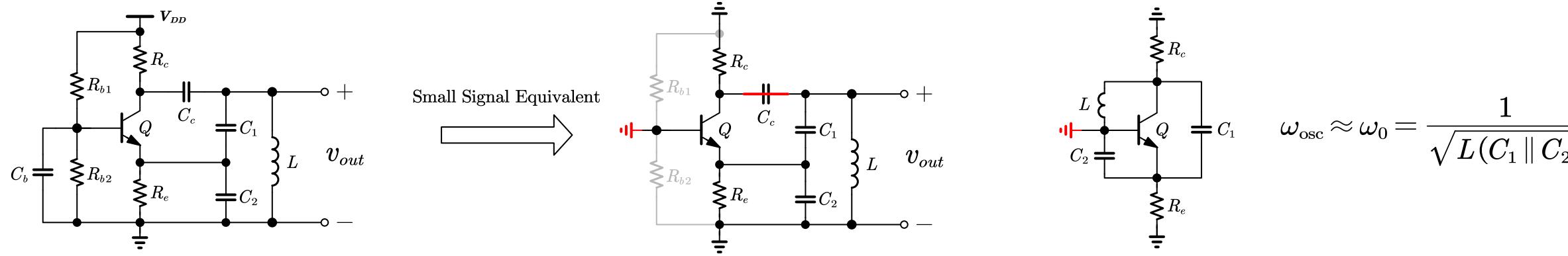



考毕兹振荡器

Colpitts Oscillator (CB)




回路总电容 $C_\Sigma = C_1 \parallel C_2$ 即为电感两端等效电容

Colpitts Oscillator (CE)

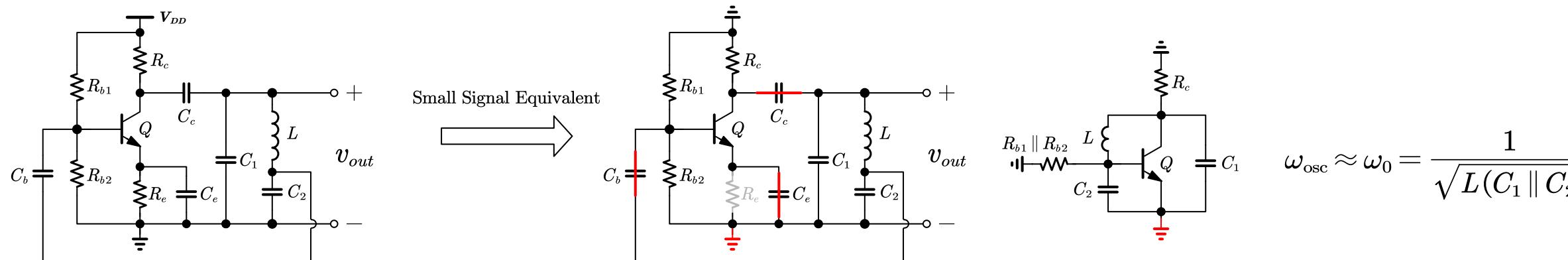

克拉泼振荡器

Clapp Oscillator (CB)

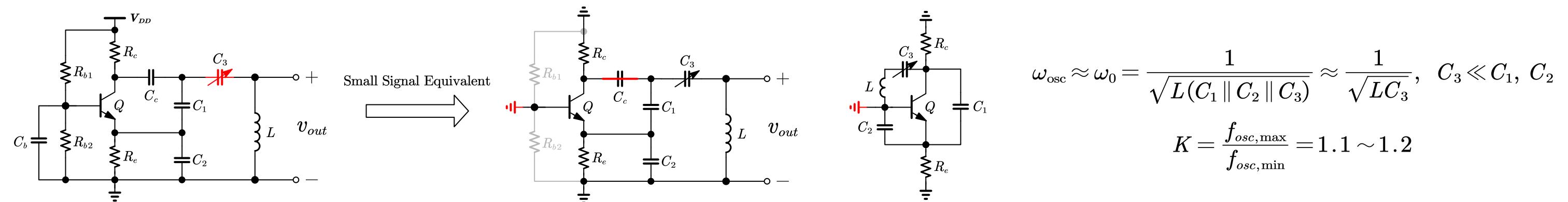

西勒振荡器

Seiler Oscillator (CB)

