

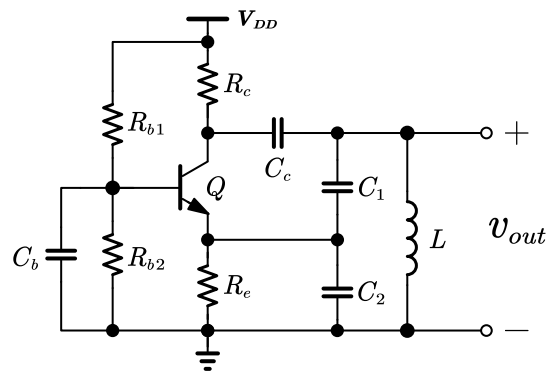
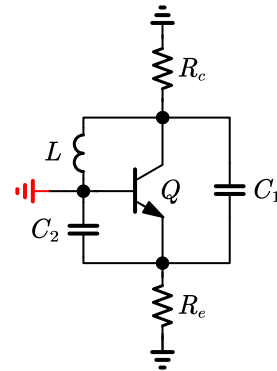


# 考毕兹振荡器

## Colpitts Oscillator (CB)

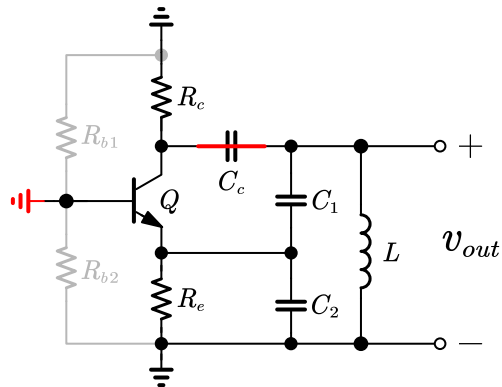


Small Signal Equivalent

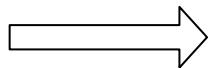




$$\omega_{\text{osc}} \approx \omega_0 = \frac{1}{\sqrt{L(C_1 \parallel C_2)}}$$

回路总电容  $C_{\Sigma} = C_1 \parallel C_2$  即为电感两端等效电容

## Colpitts Oscillator (CE)

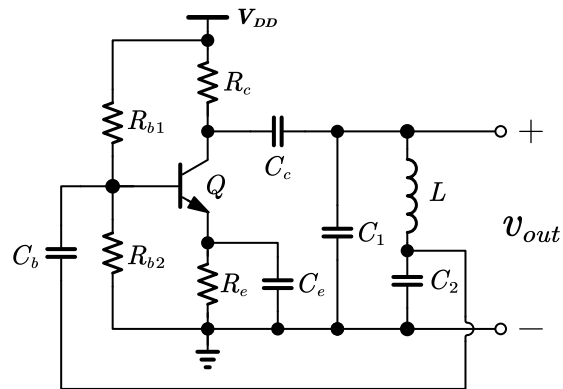

Small Signal Equivalent

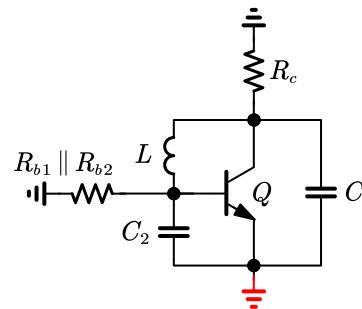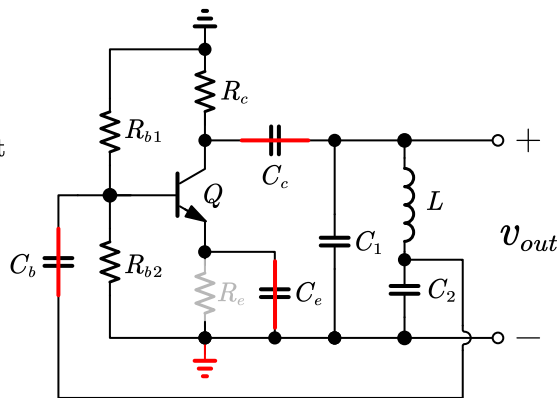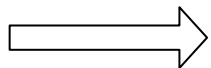

$$\omega_{\text{osc}} \approx \omega_0 = \frac{1}{\sqrt{L(C_1 \parallel C_2)}}$$